 




**題目：Multiplexers, Number and Displays**

**繳交日期：2023/07/09**






## 1. 實驗程式碼

### ◆ lab1\_1→2-to1 multiplexer

```
module LAB1_1 (SW, LEDR);  
    input [9:0] SW;  
    output [3:0] LEDR;  
  
    multiplexer_2to1 mux(SW[3:0], SW[7:4], SW[9], LEDR[3:0]);  
endmodule  
  
module multiplexer_2to1 (x, y, s, led);  
    input [3:0] x, y;  
    input s;  
    output [3:0] led;  
  
    assign led[3:0] = {{~{4{s}}}&x[3:0]}|{{4{s}}&y[3:0]};  
endmodule
```

### ◆ lab1\_2→7-segment displays

 



```
module LAB1_2 (SW, HEX0);
    input [3:0] SW;
    output [6:0] HEX0;

    seg_decoder de(SW[3:0], HEX0);
endmodule
//bcd to seg
module seg_decoder (bcd, seg);
    input [3:0] bcd;
    output [6:0] seg;
    reg [6:0] seg;

    always @(bcd) begin
        case (bcd)
            0 : seg = 7'b1000000;
            1 : seg = 7'b1111001;
            2 : seg = 7'b0100100;
            3 : seg = 7'b0110000;
            4 : seg = 7'b0011001;
            5 : seg = 7'b0010010;
            6 : seg = 7'b0000010;
            7 : seg = 7'b1111000;
            8 : seg = 7'b0000000;
            9 : seg = 7'b0010000;
            //lights out
            default : seg = 7'b1111111;
        endcase
    end
endmodule
```


◆ lab1\_3→Binary coded decimal

```
module LAB1_3 (SW, HEX0, HEX1);
    input [3:0] SW;
    output [6:0] HEX0, HEX1;

    two_digit_seg A(SW[3:0], HEX1, HEX0);
endmodule

//display two digit in seg
module two_digit_seg (bcd, seg1, seg0);
    input [3:0] bcd;
    output [6:0] seg1, seg0;

     seg_decoder de1(bcd/10, seg1);
    seg_decoder de0(bcd%10, seg0);
endmodule
```





```
//bcd to seg
module seg_decoder (bcd, seg);
    input [3:0] bcd;
    output [6:0] seg;
    reg [6:0] seg;

    always @(bcd) begin
        case (bcd)
            0 : seg = 7'b1000000;
            1 : seg = 7'b1111001;
            2 : seg = 7'b0100100;
            3 : seg = 7'b0110000;
            4 : seg = 7'b0011001;
            5 : seg = 7'b0010010;
            6 : seg = 7'b0000010;
            7 : seg = 7'b1111000;
            8 : seg = 7'b0000000;
            9 : seg = 7'b0010000;
            //lights out
            default : seg = 7'b1111111;
        endcase
    end
endmodule
```

◆ lab1\_4→Full adder


```
module LAB1_4 (SW, LEDR);
    input [9:0] SW;
    output [4:0] LEDR;

    full_adder FA(SW[3:0], SW[7:4], SW[9], LEDR[4], LEDR[3:0]);
endmodule

//4bit full adder
module full_adder (a, b, c_in, c_out, sum);
    input c_in;
    input [3:0] a, b;
    output c_out;
    output [3:0] sum;

    assign {c_out, sum} = a + b + c_in;
endmodule
```

◆ lab1\_5→Add two 1-digit BCD numbers

 




```
module LAB1 (SW, HEX0, HEX1, HEX2, HEX3, HEX4, HEX5, LEDR);
    input [8:0] SW;
    output [6:0] HEX0, HEX1, HEX2, HEX3, HEX4, HEX5;
    output [9:0] LEDR;
    reg [9:0] LEDR;
    wire [3:0] sum;
    wire [4:0] result;
    wire c_out;
    |
    //display A and B in seg
    two_digit_seg A(SW[7:4], HEX3, HEX2);
    two_digit_seg B(SW[3:0], HEX1, HEX0);

    //display sum result in seg
    full_adder FA(SW[7:4], SW[3:0], SW[8], c_out, sum);
    assign result = {c_out, sum};
    two_digit_seg result_de(result, HEX5, HEX4);

    //LEDR9 turn on when A or B is greater than 9
    always @(*) begin
        if(SW[7:4] > 9 || SW[3:0] > 9) begin
            LEDR[9] = 1'b1;
        end
        else begin
            LEDR[9] = 1'b0;
        end
    end
end

endmodule
```

 



```
//bcd to seg
module seg_decoder (bcd, seg);
    input [3:0] bcd;
    output [6:0] seg;
    reg [6:0] seg;

    always @(bcd) begin
        case (bcd)
            0 : seg = 7'b1000000;
            1 : seg = 7'b1111001;
            2 : seg = 7'b0100100;
            3 : seg = 7'b0110000;
            4 : seg = 7'b0011001;
            5 : seg = 7'b0010010;
            6 : seg = 7'b0000010;
            7 : seg = 7'b1111000;
            8 : seg = 7'b0000000;
            9 : seg = 7'b0010000;
            //lights out
            default : seg = 7'b1111111;
        endcase
    end
endmodule
```

```
//display two digit in seg
module two_digit_seg (bcd, seg1, seg0);
    input [4:0] bcd;
    output [6:0] seg1, seg0;


    seg_decoder de1(bcd/10, seg1);
    seg_decoder de0(bcd%10, seg0);
endmodule
```

```
//4bit full adder
module full_adder (a, b, c_in, c_out, sum);
    input c_in;
    input [3:0] a, b;
    output c_out;
    output [3:0] sum;


    assign {c_out, sum} = a + b + c_in;
endmodule
```

## 2. 實驗結果



### ◆ lab1\_1

 



 


◆ lab1\_2

  

◆ lab1\_3






 


◆ lab1\_4






 

◆ lab1\_5

 






   

### 3. RTL 佈局


◆ lab1\_1



 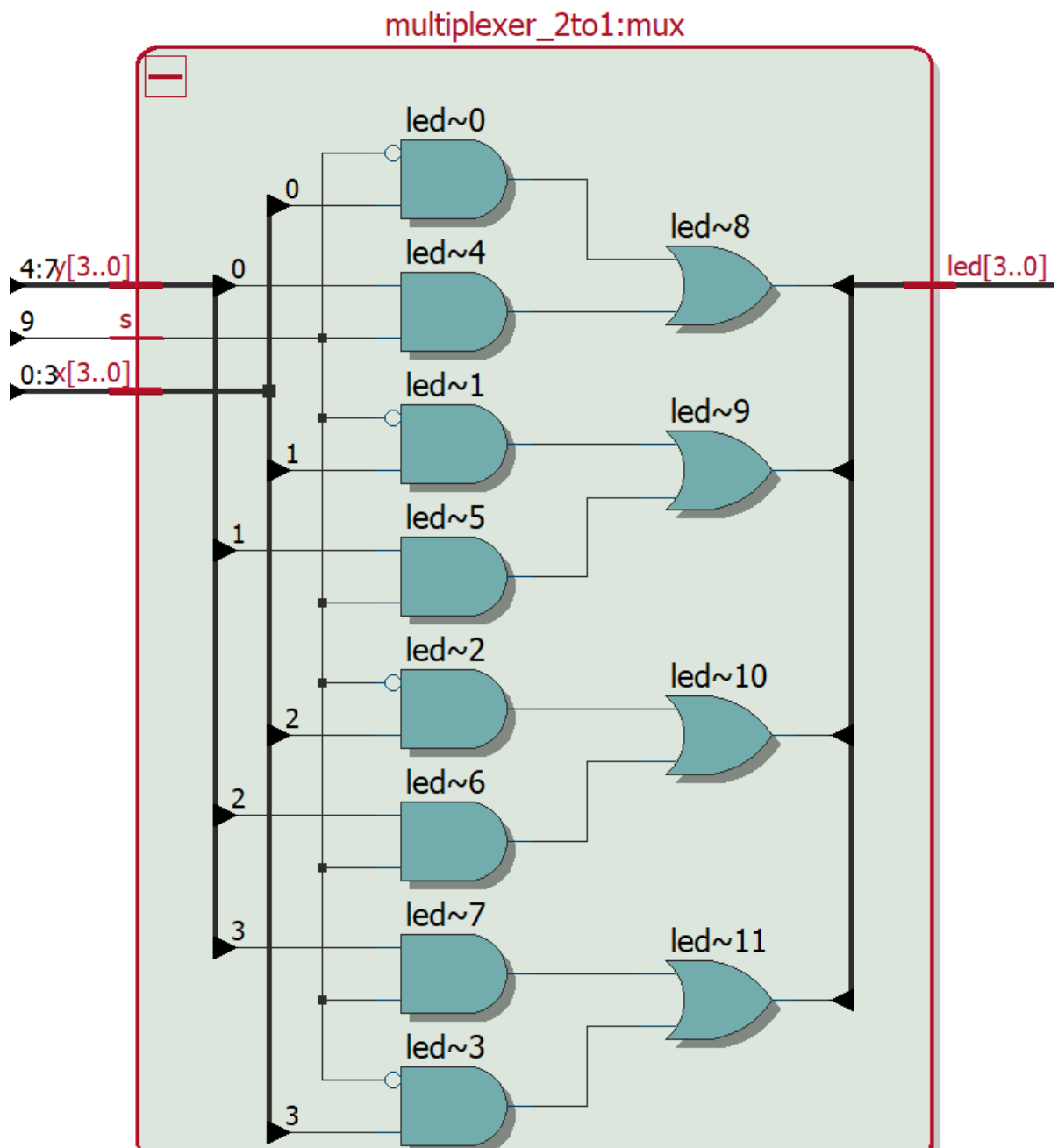 







◆ lab1\_2

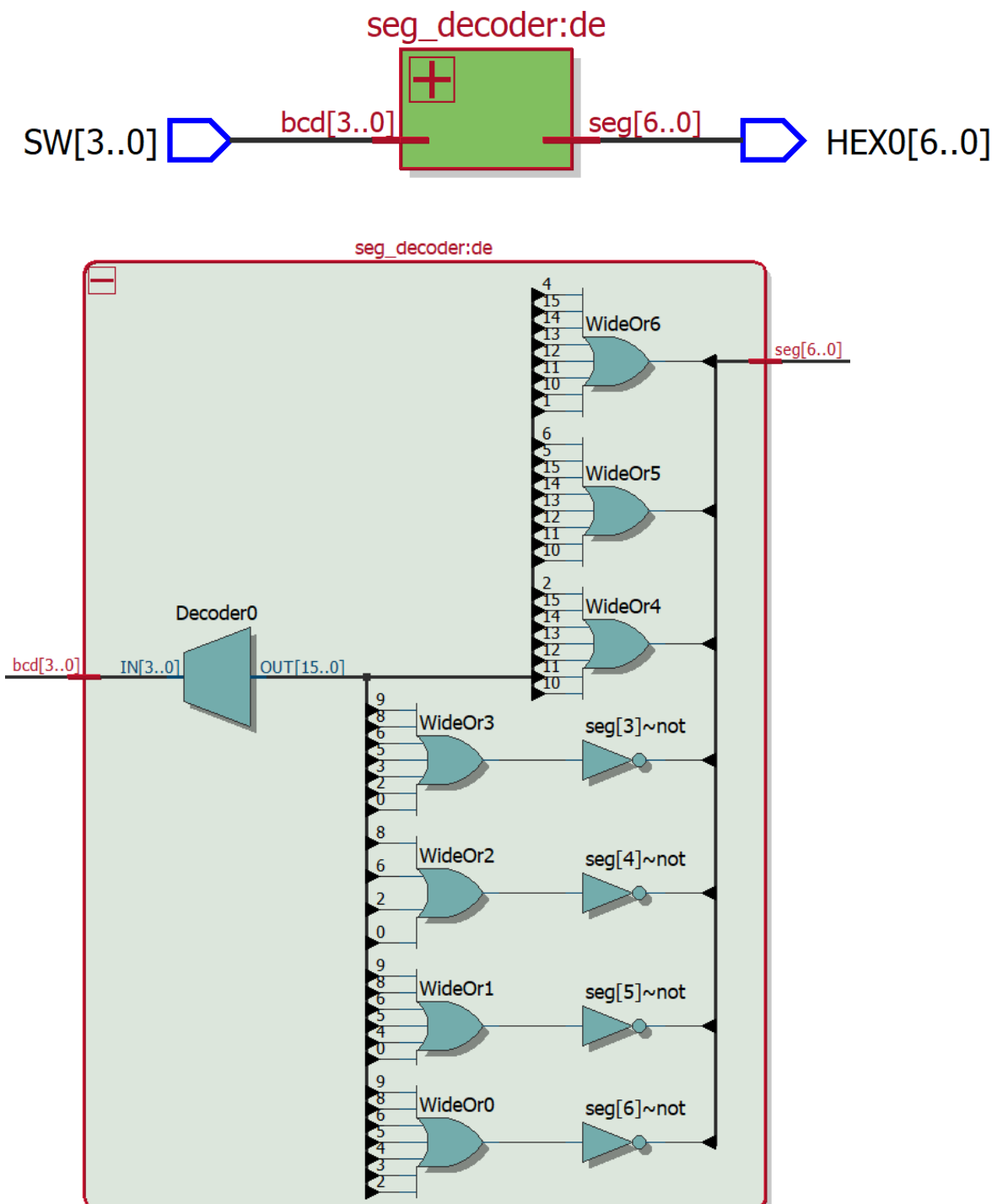


◆ lab1\_3



 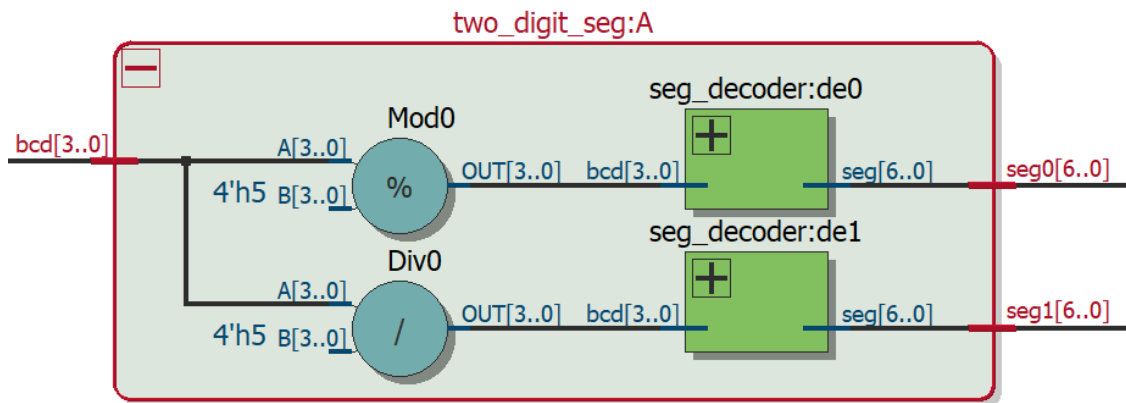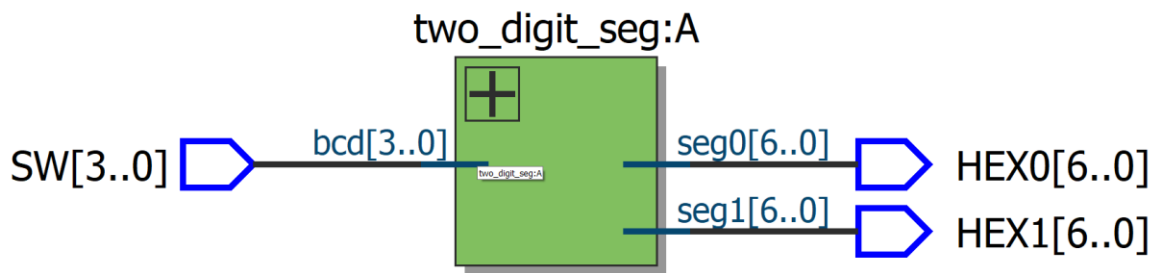


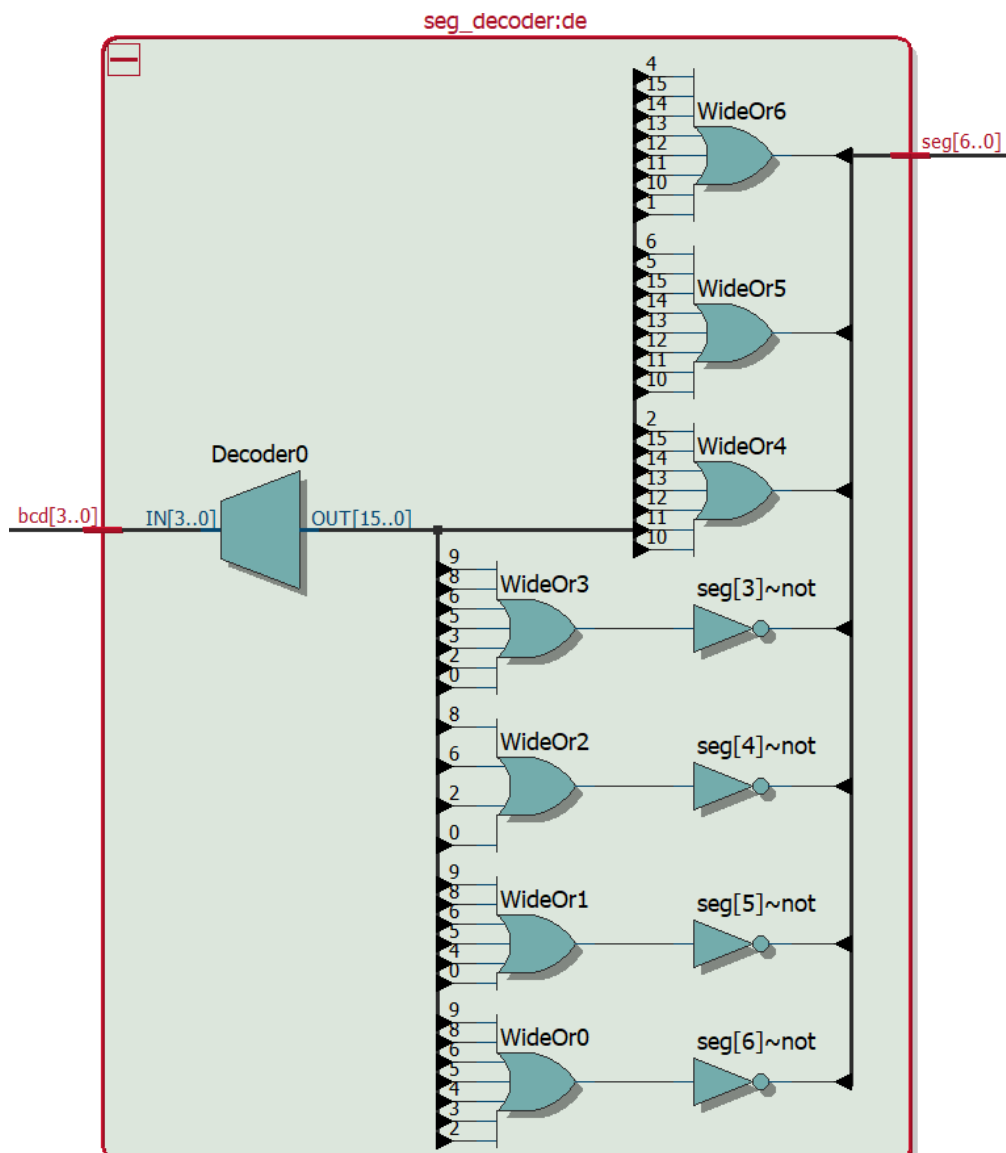


◆ lab1\_4

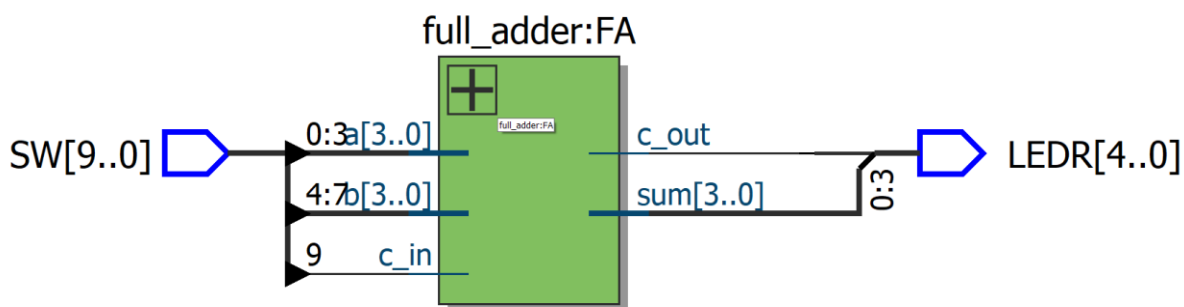





 

◆ lab1\_5

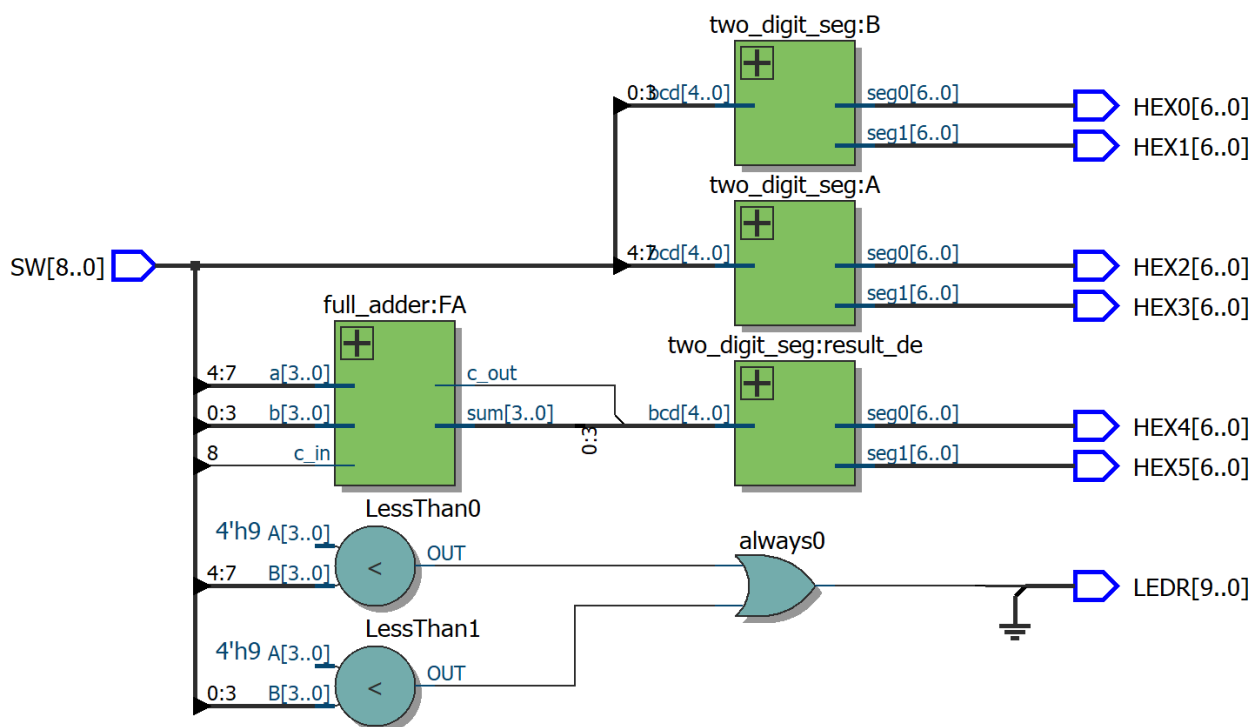


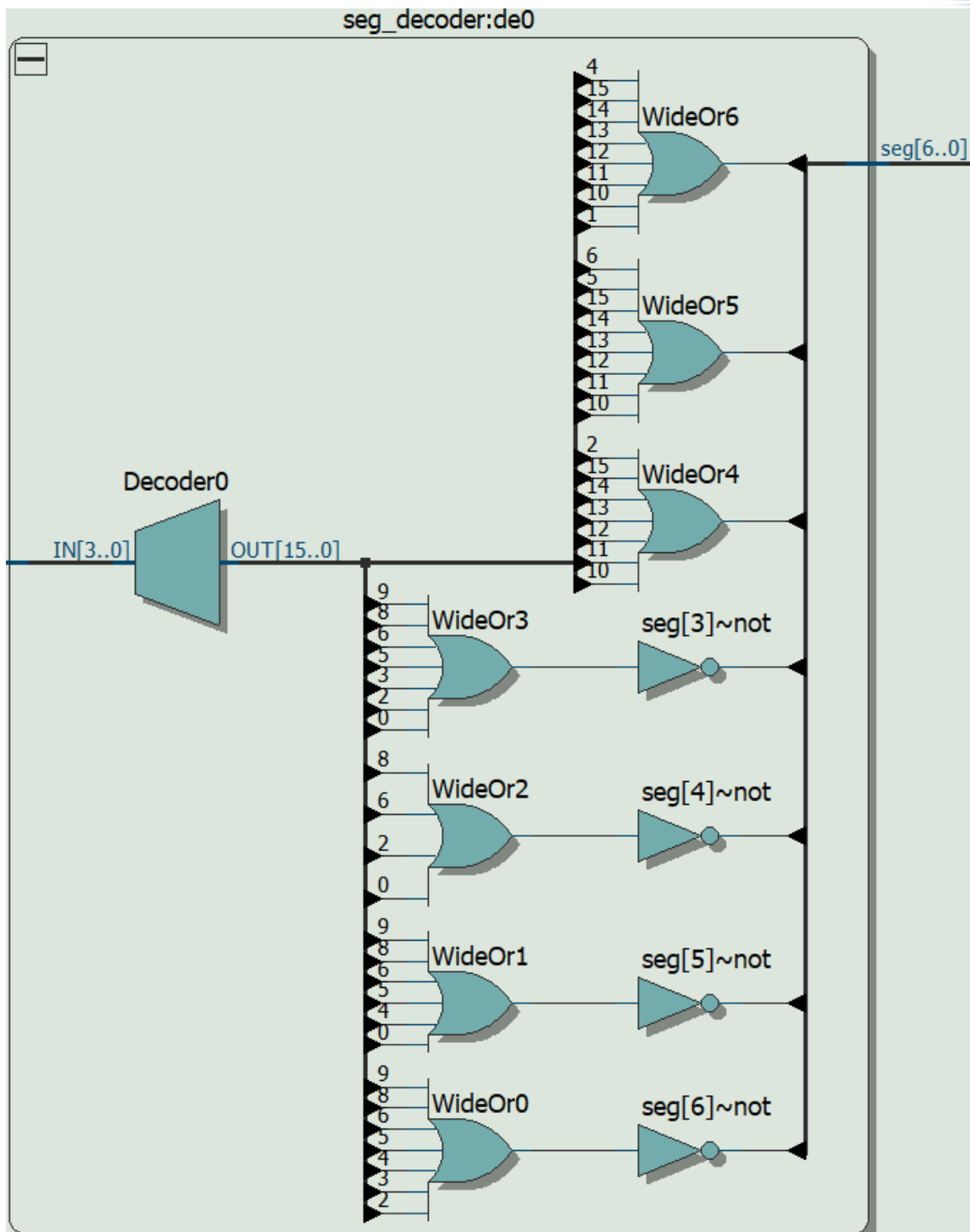

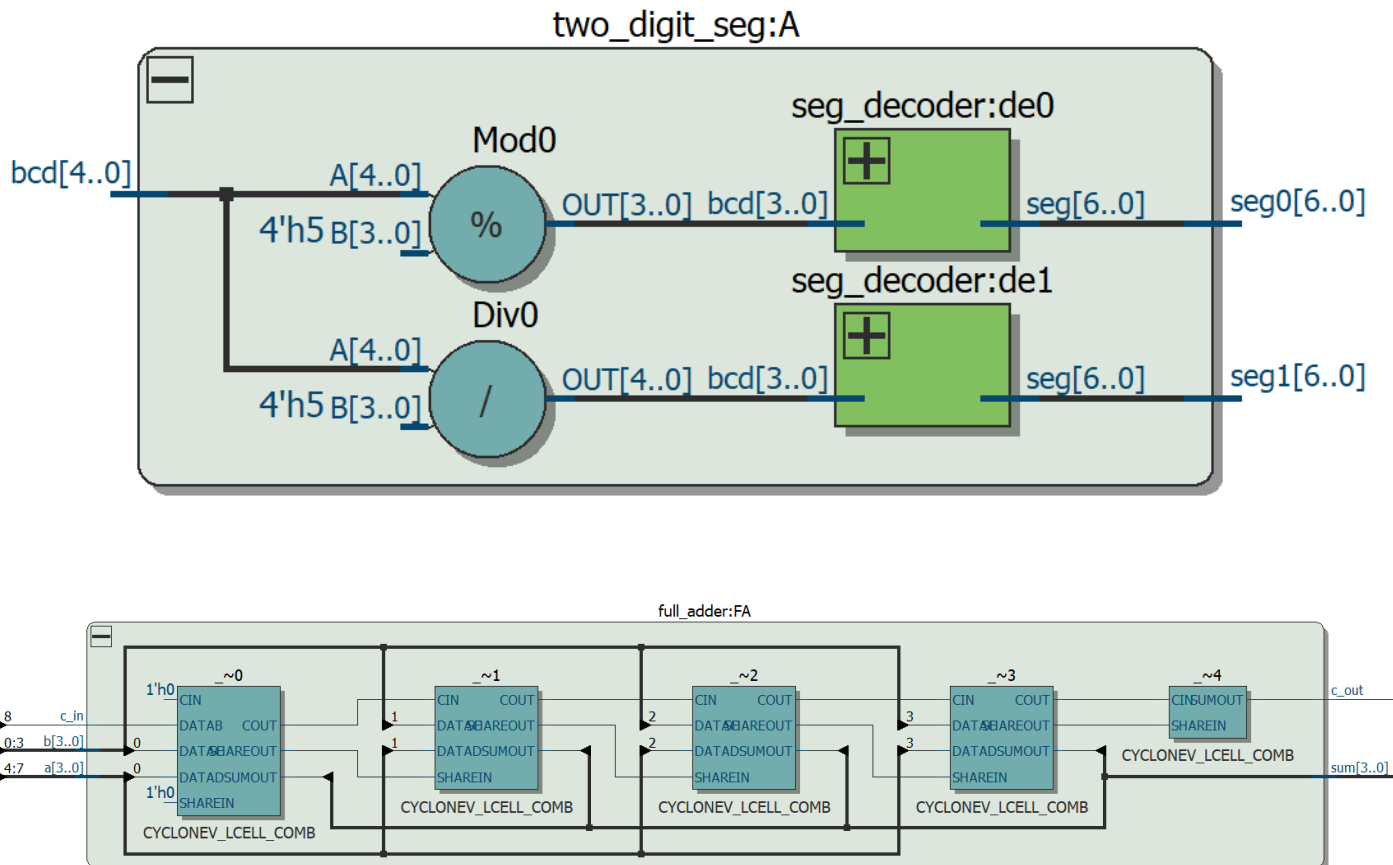
 
#### 4. 問題與討論

- ✚ reg 和 wire 類似 C/C++ 的變數，但是有位寬，預設是一位元。input, output 和 inout 預設是 wire，要改成 reg 需要另外宣告。
- ✚ begin end 相當於 C/C++ 的 {}，可執行多行指令，內部只能放 reg。
- ✚ 賦值(連接線路)時，wire 要使用 assign，而 reg 不用。
- ✚ 一般來說，只有在時序電路(always block 的敏感列表中是 clock 形式)，reg 是 register，可以重複賦值，不然還是和 wire 一樣是 net(一條導線)，不能重複賦值。
- ✚ always block：@後面放列表訊號，這些訊號改變才會觸發 block，沒有@代表會一直執行 block
  - \*代表 block 內所有輸入訊號
  - 敏感列表只要沒有 clock 就是組合邏輯電路
- ✚ assign 訊號只要右端訊號改變就會執行該語句的計算，always block 只要敏感變量訊號改變就會執行該 block







不能在 `always block` 裡面初始化 module

{ } 內可以串接不同變數，串接順序由右至左為 LSB 到 MSB，在 `full adder` 有使用此技巧

