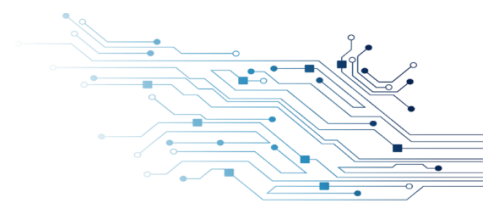




題目：Time-of-day clock





1. 實驗程式碼


```
module LAB2 (SW, CLOCK_50, HEX0, HEX1, HEX2, HEX3, HEX4, HEX5);
    input [9:0] SW;
    input CLOCK_50;
    output [6:0] HEX0, HEX1, HEX2, HEX3, HEX4, HEX5;
    wire [5:0] sec;
    wire [7:0] hour, min;

    timer Timer (CLOCK_50, SW[8], SW[9], SW[7:0], hour, min, sec);

    two_digit_seg sec_display(sec, HEX1, HEX0);
    two_digit_seg min_display(min, HEX3, HEX2);
    two_digit_seg hour_display(hour, HEX5, HEX4);
endmodule


module timer (clk, set, select, setting_time, hour, min, sec);
    input clk, set, select;
    input [7:0] setting_time;
    output [7:0] hour, min;
    output [5:0] sec;
    reg [7:0] hour, min;
    reg [5:0] sec;
    reg [25:0] sec_count;
    integer flag = 0; //for the purpose of posedge of set
```

```
always @(posedge clk) begin
    //clock 00:00:00 ~ 23:59:59
    if(sec_count >= 50000000) begin
        sec_count = 0;
        sec = sec + 1;
        if(sec >= 60) begin
            sec = 0;
            min = min + 1;
            if(min >= 60) begin
                min = 0;
                hour = hour + 1;
                if(hour >= 24) begin
                    hour = 0;
                    min = 0;
                    sec = 0;
                end
            end
        end
    end
    else begin
        sec_count = sec_count + 1;
    end
end
```

 



```
//set hour or min
if(set == 1) begin
    if(flag == 0) begin
        flag = 1;
        if(select == 1) begin
            //setting hour time must be less than 24
            if(setting_time > 23)
                hour = 23;
            else begin
                hour = setting_time;
            end
        end
    end
    else begin
        //setting minute time must be less than 60
        if(setting_time > 59)
            min = 59;
        else begin
            min = setting_time;
        end
    end
end
end
else begin
    flag = 0;
end
end
endmodule
```

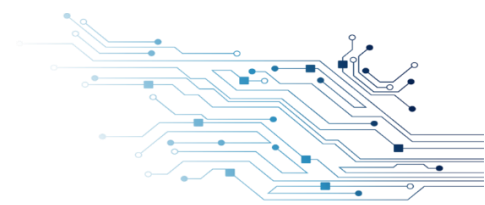




```
//bcd to seg
module seg_decoder (bcd, seg);
    input [7:0] bcd;
    output [6:0] seg;
    reg [6:0] seg;



    always @(bcd) begin
        case (bcd)
            0 : seg = 7'b1000000;
            1 : seg = 7'b1111001;
            2 : seg = 7'b0100100;
            3 : seg = 7'b0110000;
            4 : seg = 7'b0011001;
            5 : seg = 7'b0010010;
            6 : seg = 7'b0000010;
            7 : seg = 7'b1111100;
            8 : seg = 7'b0000000;
            9 : seg = 7'b0010000;
            //lights out
            default : seg = 7'b1111111;
        endcase
    end
endmodule

//display two digit in seg
module two_digit_seg (bcd, seg1, seg0);
    input [7:0] bcd;
    output [6:0] seg1, seg0;


    seg_decoder de1(bcd/10, seg1);
    seg_decoder de0(bcd%10, seg0);
endmodule
```



2. 實驗結果

 


  


3. RTL 佈局

 

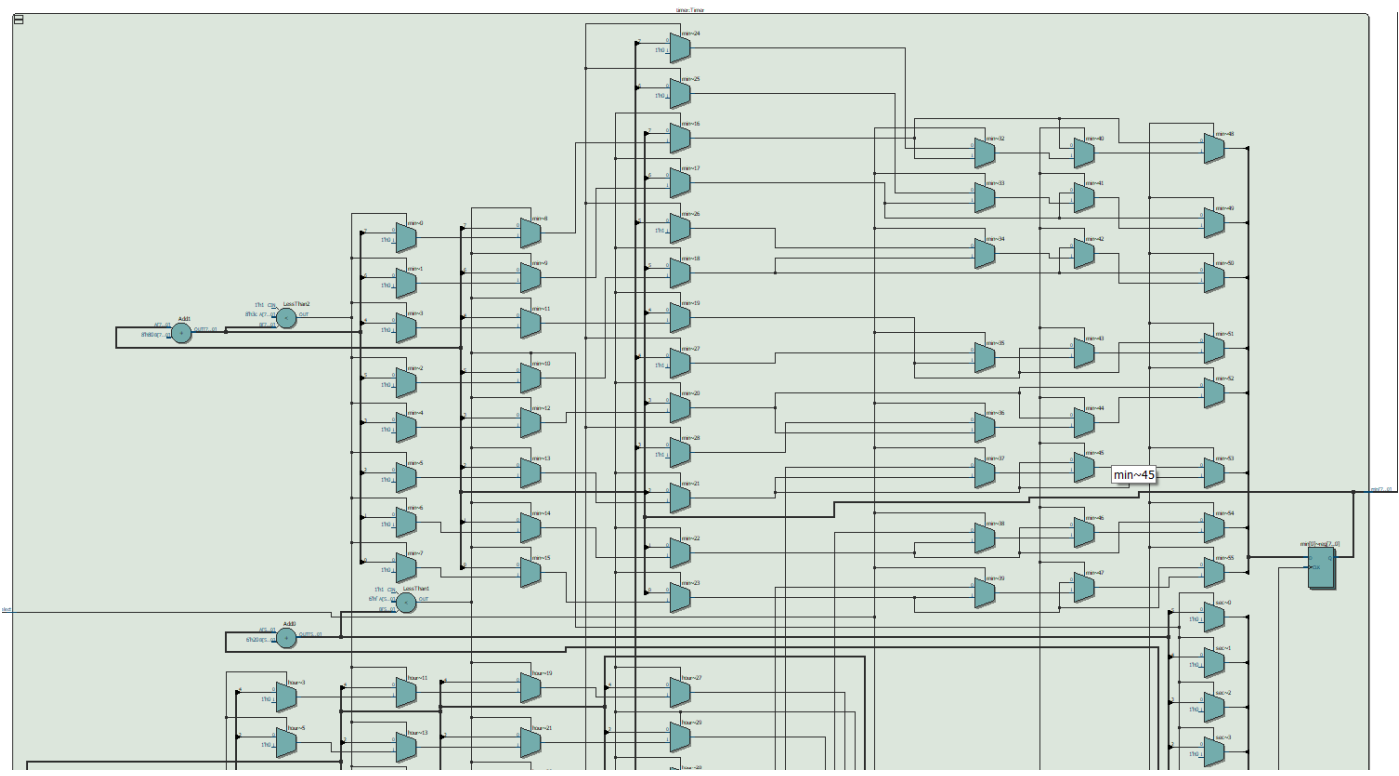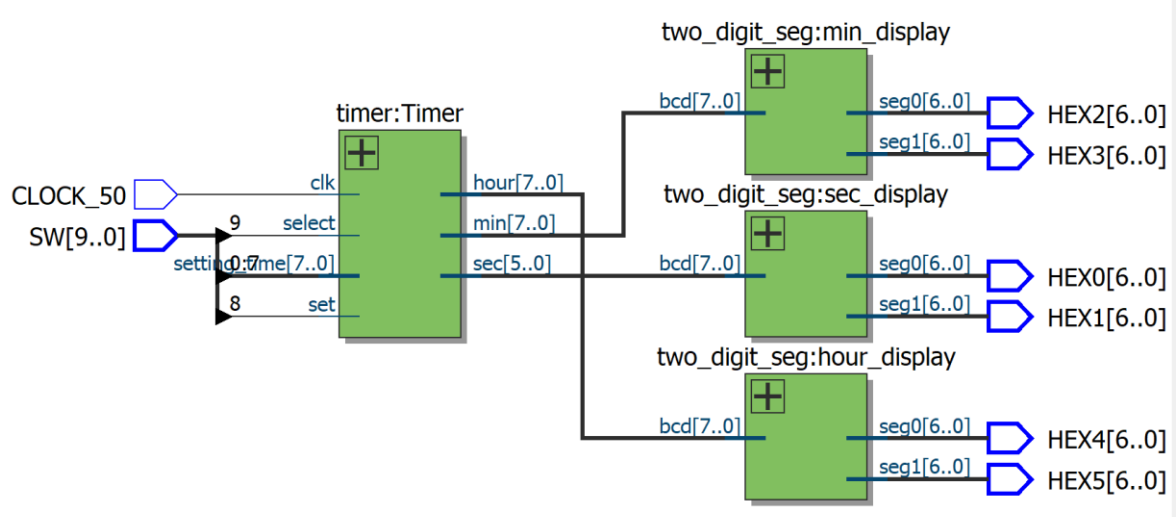


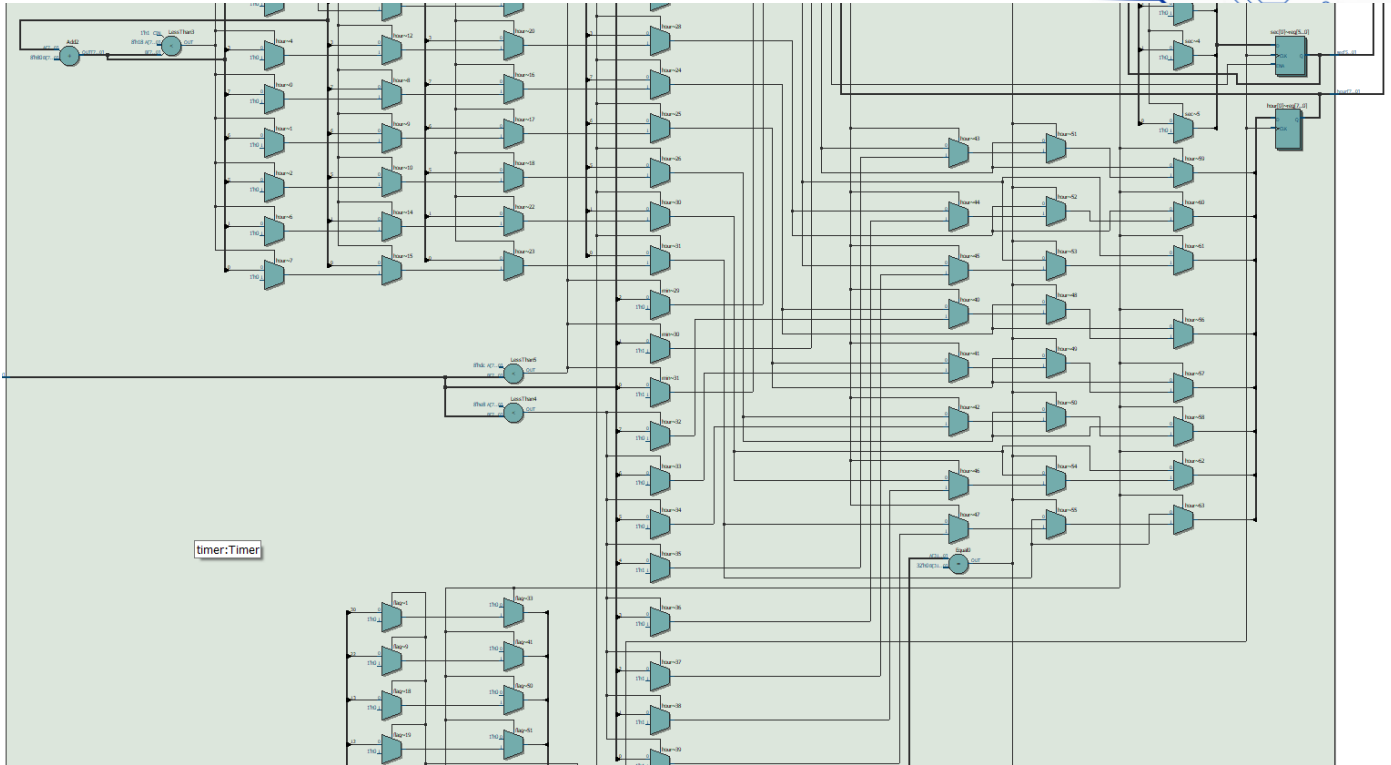


 







two_digit_seg:sec_display

 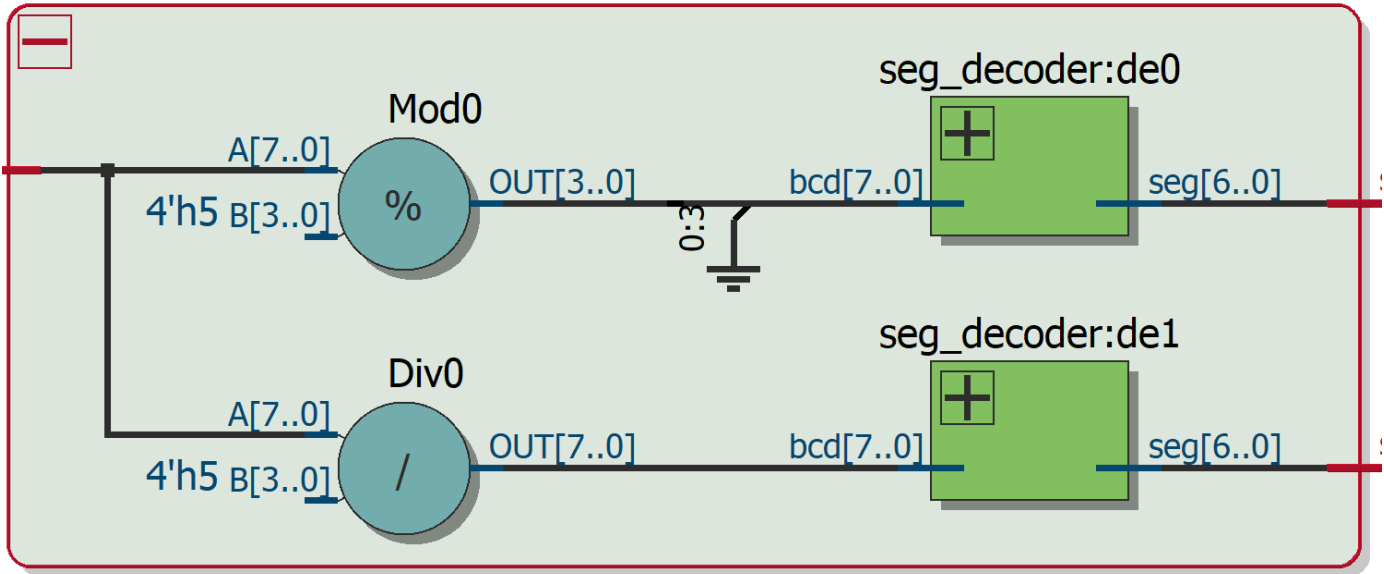

 

4. 問題與討論

- 不能在不同的 always block 對相同變數賦值。

 



- always block 的敏感列表如果有兩個 edge 訊號，其中一個必須寫在 if 判斷式裡面，而且必須針對 pos 或是 neg 去做匹配(neg 要加~，pos 不用加)。如果是三個依此類推，並用 if else_if else。沒寫在條件判斷式的訊號就是 clock，剩餘的都是非同步訊號。
- 當有兩個非同步訊號輸入都有效時，就會有優先級的問題，擺在 if 的那個最優先。
- 通常非同步訊號都用作 set 或 reset 用途，reset 的功能為讓電路訊號通電後進入一個穩定狀態，以免進入隨機狀態而無法正常工作。
- integer 為 32 位元的有號數，用來當作 for loop 計數，for loop 可以複製電路以精簡程式碼，例如 32 位元加法器可以用一行加法器程式碼配合迴圈 32 次完成，效果是等價。除此之外，不要使用 integer，要用 wire 或 reg。

