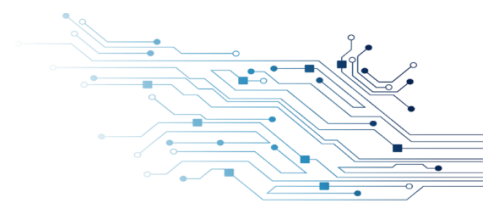




題目：A Simple Processor





1. 實驗程式碼

```
module LAB6 (KEY, LEDR, HEX5, HEX4, HEX3, HEX2, HEX1, HEX0);
    input [2:0] KEY;
    output reg [7:0] LEDR;
    output [6:0] HEX5, HEX4, HEX3, HEX2, HEX1, HEX0;
    wire [4:0] addr;
    wire [7:0] instruction, R1, R0;

    rom1 ROM(
        .address(addr),
        .clock(~KEY[1]),
        .q(instruction));


    always @(posedge ~KEY[2]) begin
        LEDR = instruction;
    end

    Program_Counter PC(~KEY[1], KEY[0], addr);
    Processor Proc(instruction, KEY[0], ~KEY[2], R1, R0);
    two_digit_seg R0_display(R0, HEX3, HEX2);
    two_digit_seg R1_display(R1, HEX1, HEX0);
    two_digit_seg instruction_display(instruction, HEX5, HEX4);

endmodule
```

```
module Program_Counter (clk, Resetn, address);
    input clk, Resetn;
    output reg [4:0] address;

     always @(posedge clk or negedge Resetn) begin
        if(~Resetn) begin
            address = 0;
        end
        else begin
            if(address >= 32) begin
                address = 0;
            end
            else begin
                address = address + 1;
            end
        end
    end
endmodule
```






```
module Processor (DIN, Resetn, clk, R1, R0);
    input [7:0] DIN;
    input Resetn, clk;
    output [7:0] R1, R0;
    reg [7:0] register[0:7];
    reg flag = 0;
    reg [2:0] index;
    integer i;
    parameter mv = 2'b00, mvi = 2'b01, add = 2'b10, sub = 2'b11;

    assign R0 = register[0];
    assign R1 = register[1];

    always @(posedge clk or negedge Resetn) begin
        if(~Resetn) begin
            for(i = 0; i < 8; i = i + 1)
                register[i] <= 0;
        end
        else begin
            if(flag) begin
                register[index] = DIN;
                flag = 0;
            end
            else begin
                case (DIN[7:6])
                    mv:
                        begin
                            register[DIN[5:3]] = register[DIN[2:0]];
                            flag = 0;
                        end
                end
            end
        end
    end
end
```

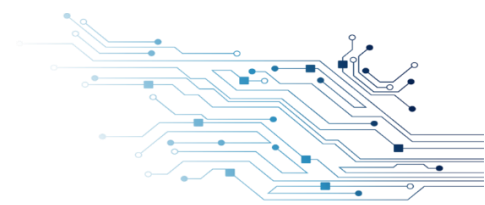




```
mvi:
begin
    index = DIN[5:3];
    flag = 1;
end
add:
begin
    register[DIN[5:3]] = register[DIN[5:3]] + register[DIN[2:0]];
    flag = 0;
end
sub:
begin
    register[DIN[5:3]] = register[DIN[5:3]] - register[DIN[2:0]];
    flag = 0;
end
endcase
end
end
end
endmodule
```

```
//bch to seg
module seg_decoder (bch, seg);
    input [3:0] bch;
    output reg [6:0] seg;

    always @(bch) begin
        case (bch)
            0 : seg = 7'b1000000;
            1 : seg = 7'b1111001;
            2 : seg = 7'b0100100;
            3 : seg = 7'b0110000;
            4 : seg = 7'b0011001;
            5 : seg = 7'b0010010;
            6 : seg = 7'b0000010;
            7 : seg = 7'b1111000;
            8 : seg = 7'b0000000;
            9 : seg = 7'b0010000;
            10 : seg = 7'b0001000; //A
            11 : seg = 7'b0000011; //b
            12 : seg = 7'b1000110; //C
            13 : seg = 7'b0100001; //d
            14 : seg = 7'b0000110; //E
            15 : seg = 7'b0001110; //F
            //lights out
            default : seg = 7'b1111111;
        endcase
    end
endmodule
```



 











```
//display two digit in seg
module two_digit_seg (num, seg1, seg0);
    input [7:0] num;
    output [6:0] seg1, seg0;


    seg_decoder de1(num[7:4], seg1);
    seg_decoder de0(num[3:0], seg0);
endmodule
```

2. 實驗結果

   


 


      

 



3. RTL 佈局





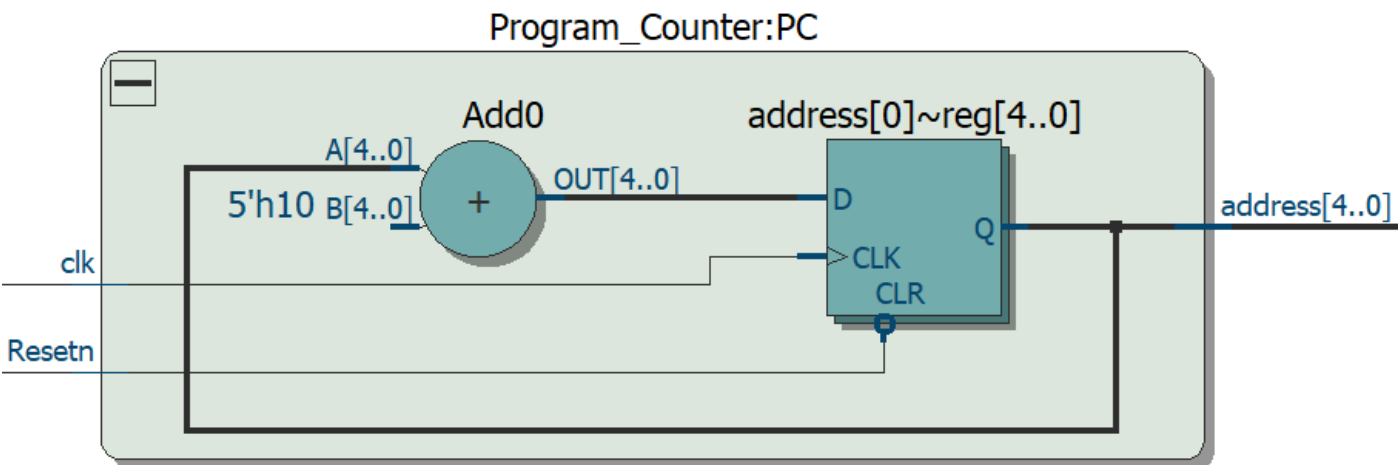
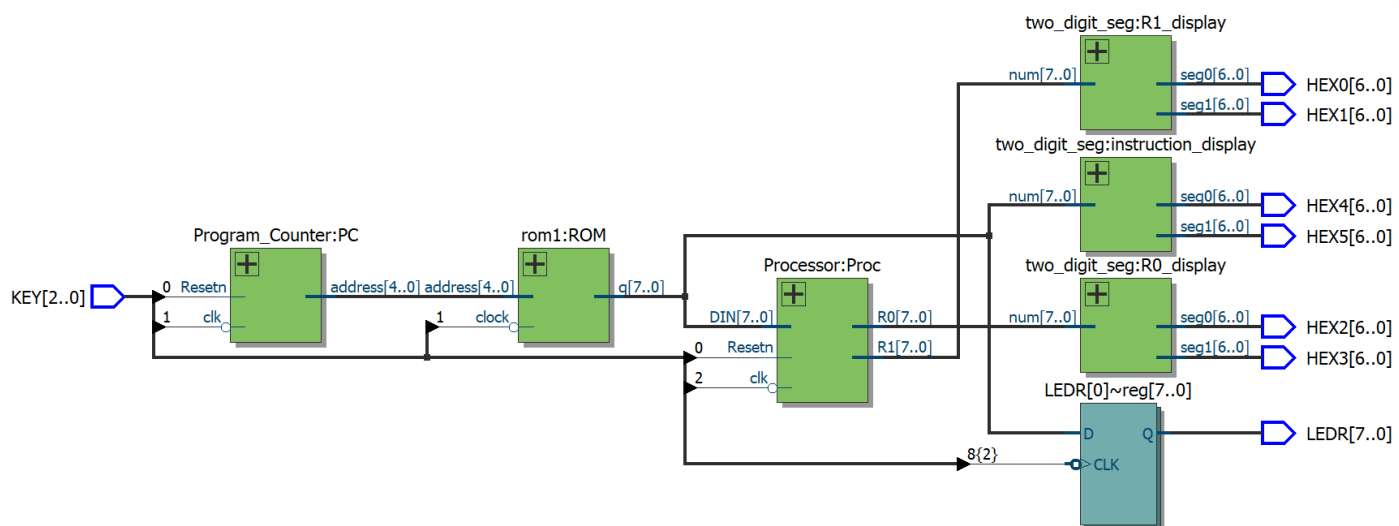






Processor

 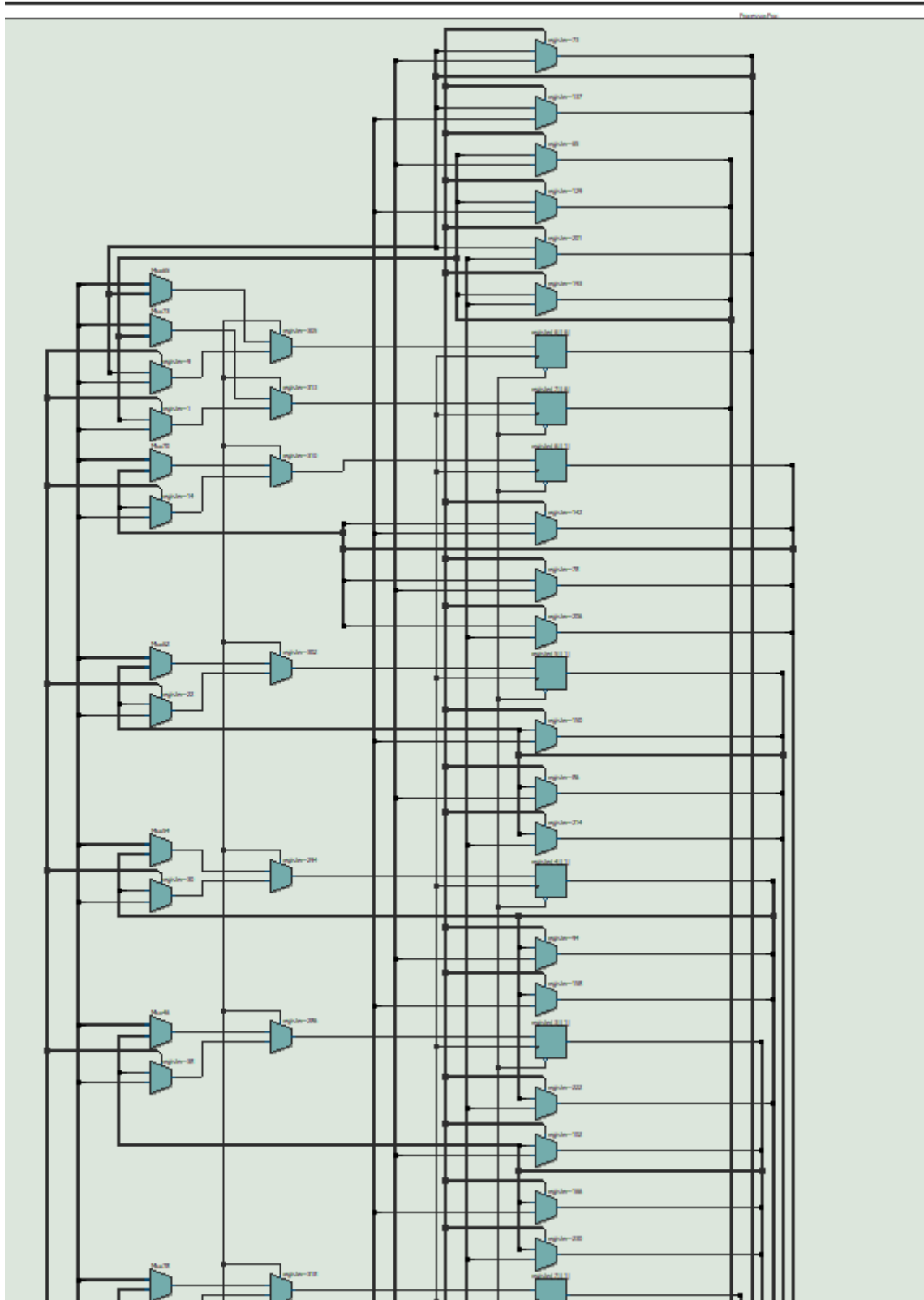

 

   

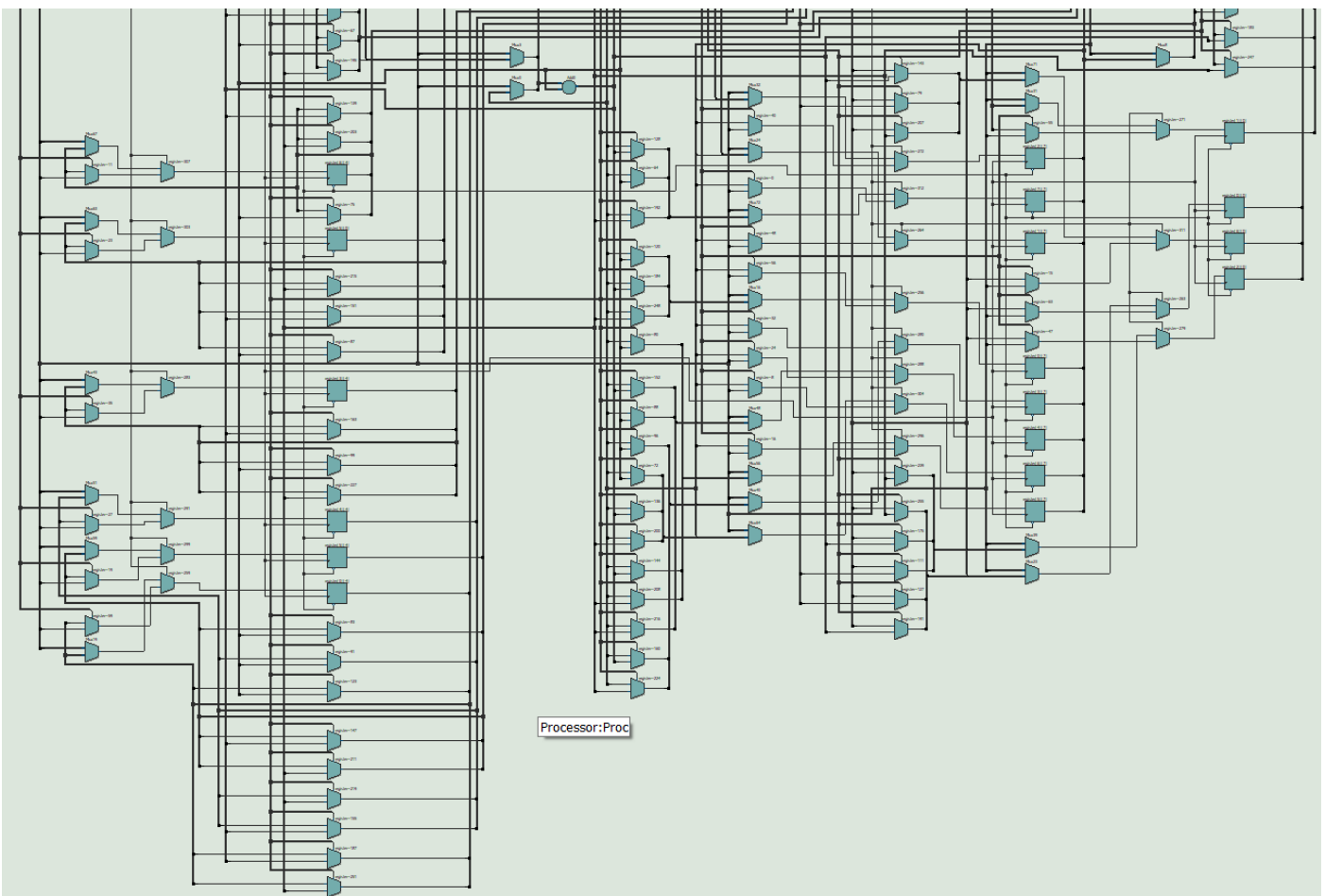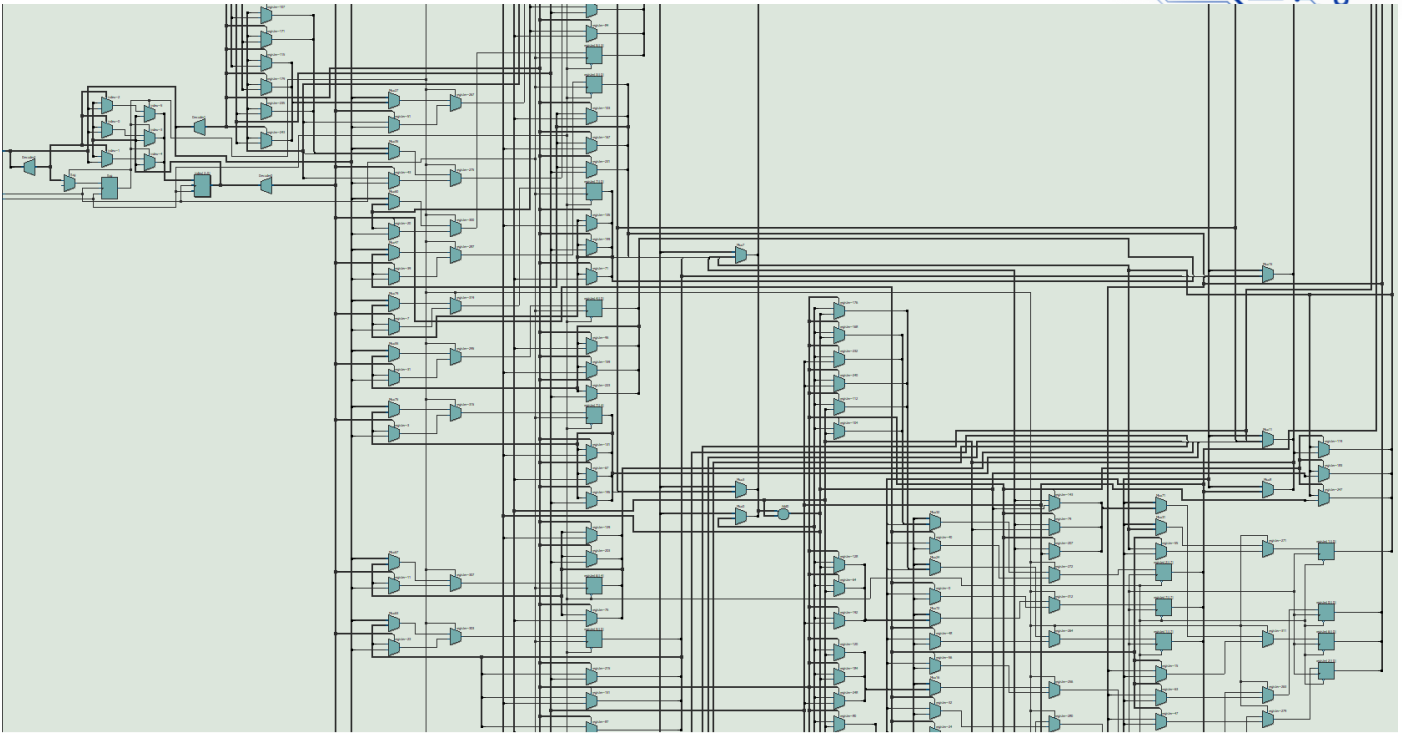

4. 問題與討論

- 由於 LEDR 是配合 PClock，所以我將 LEDR 宣告為 reg，在 PClock posedge 才觸發，而不是直接連接 DIN。





- Processor 內部有八個暫存器儲存指令計算的結果，其中把 0 號和 1 號暫存器拉出去作為輸出，flag 為判斷是否為 mvi 指令。

